



Universidade de Brasília - UnB
Departamento de Engenharia Eletrica - ENE

Pré-relatório Experimento 4
Implementação de circuitos combinacionais com
multiplexadores



Carlos Eduardo Taborda Lottermann
180041509

Prof. Luís Fernando Ramos Molinaro


Brasília, DF
2019

Desenhos esquemáticos:

Visto 1:

 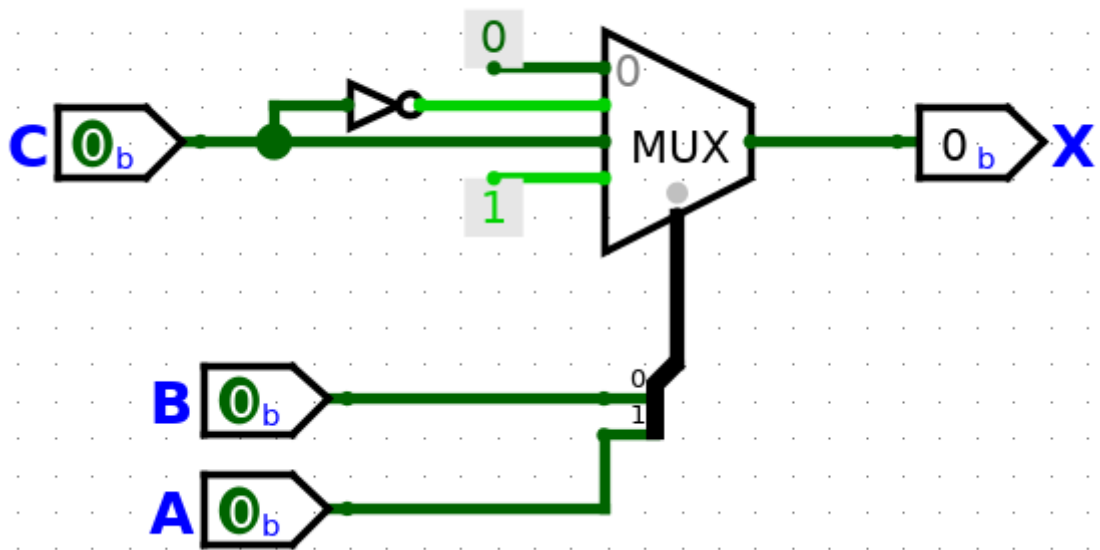

Visto 2:

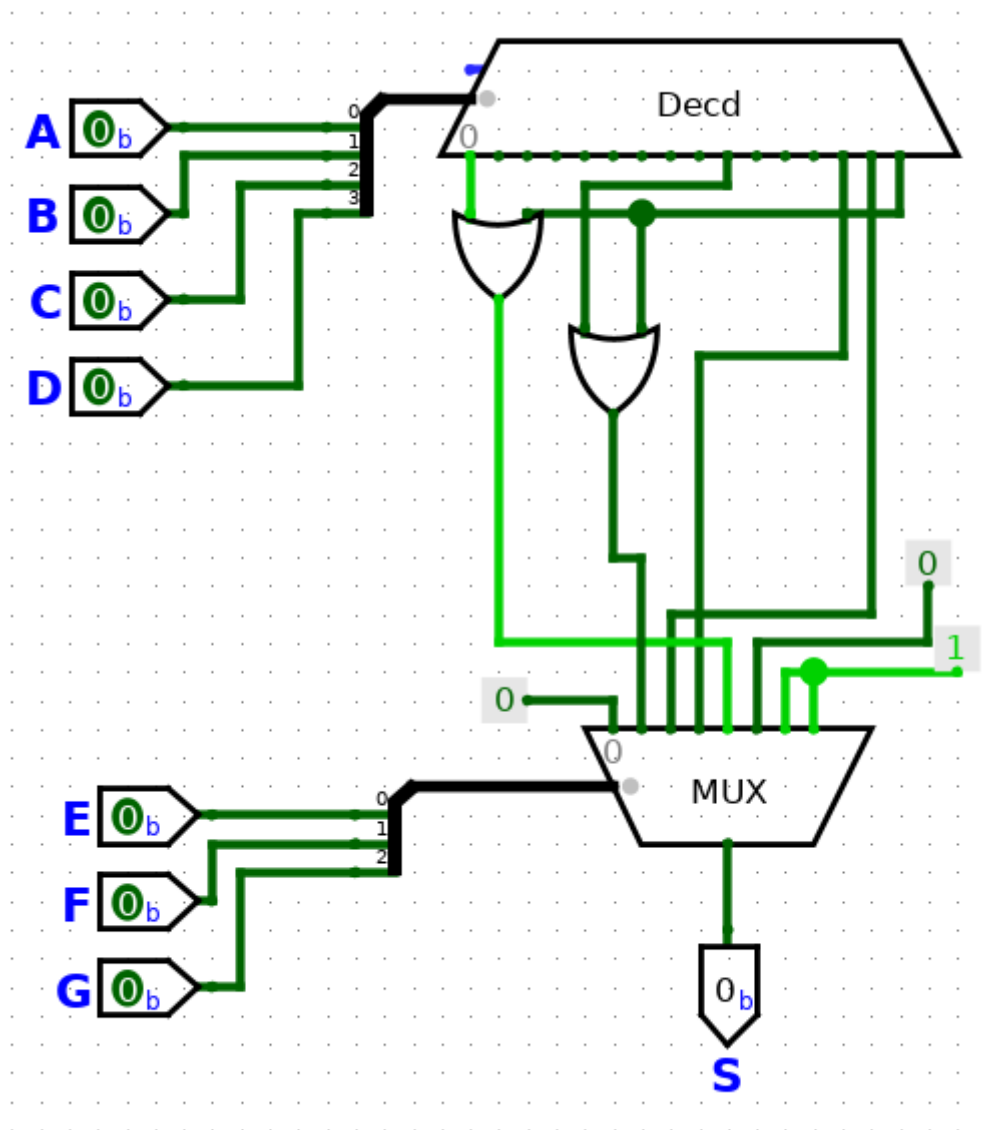

Código em VHDL do 1º visto:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Visto_1 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          X : out STD_LOGIC;
          Y : out STD_LOGIC);
end Visto_1;

architecture Visto_1_op of Visto_1 is

    component MUX is
        Port ( S : in  STD_LOGIC_VECTOR (1 downto 0);
              D : in  STD_LOGIC_VECTOR (3 downto 0);
              Y : out STD_LOGIC);
    end component;

    signal X_sel : STD_LOGIC_VECTOR (1 downto 0);
    signal X_in  : STD_LOGIC_VECTOR (3 downto 0);
    signal Y_sel : STD_LOGIC_VECTOR (1 downto 0);
    signal Y_in  : STD_LOGIC_VECTOR (3 downto 0);

begin

    X_sel(0) <= B;
    X_sel(1) <= A;

    X_in(0) <= '0';
    X_in(1) <= not C;
    X_in(2) <= C;
    X_in(3) <= '1';
    Xu: MUX port map(X_sel,X_in, X);
```

```
Y_sel(0) <= B;  
Y_sel(1) <= A;  
  
Y_in(0) <= '1';  
Y_in(1) <= '0';  
Y_in(2) <= not C;  
Y_in(3) <= C;  
  
Yu: MUX port map(Y_sel,Y_in,Y);  
  
end Visto_1_op;
```

Arquivo UCF do 1º visto:

```
NET "A" LOC = "K3";  
NET "B" LOC = "L3";  
NET "C" LOC = "P11";  
NET "X" LOC = "M11";  
NET "Y" LOC = "M5";
```

Código VHDL do 2º visto:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Visto_2 is
    Port ( A : in  STD_LOGIC;
          B : in  STD_LOGIC;
          C : in  STD_LOGIC;
          D : in  STD_LOGIC;
          E : in  STD_LOGIC;
          F : in  STD_LOGIC;
          G : in  STD_LOGIC;
          S : out STD_LOGIC);
end Visto_2;

architecture Visto_2_op of Visto_2 is

    component MUX_8 is
        Port ( S : in  STD_LOGIC_VECTOR (2 downto 0);
              D : in  STD_LOGIC_VECTOR (7 downto 0);
              Y : out STD_LOGIC);
    end component;

    component Decoder is
        Port ( A : in  STD_LOGIC_VECTOR (3 downto 0);
              Y : out STD_LOGIC_VECTOR (15 downto 0));
    end component;

    signal Decoder_sel : STD_LOGIC_VECTOR (3 downto 0);
    signal Decoder_out : STD_LOGIC_VECTOR (15 downto 0);

    signal MUX_sel : STD_LOGIC_VECTOR (2 downto 0);
    signal MUX_in : STD_LOGIC_VECTOR (7 downto 0);
    signal MUX_out : STD_LOGIC;
```

```
begin
```

```
Decoder_sel(0) <= A;
```

```
Decoder_sel(1) <= B;
```

```
Decoder_sel(2) <= C;
```

```
Decoder_sel(3) <= D;
```

```
Dec: Decoder port map(Decoder_sel,Decoder_out);
```

```
MUX_sel(0) <= E;
```

```
MUX_sel(1) <= F;
```

```
MUX_sel(2) <= G;
```

```
MUX_in(0) <= '0';
```

```
MUX_in(1) <= Decoder_out(9) or Decoder_out(15);
```

```
MUX_in(2) <= Decoder_out(14);
```

```
MUX_in(3) <= Decoder_out(13);
```

```
MUX_in(4) <= Decoder_out(1) or Decoder_out(15);
```

```
MUX_in(5) <= '0';
```

```
MUX_in(6) <= '1';
```

```
MUX_in(7) <= '1';
```

```
M: MUX_8 port map(MUX_sel,MUX_in,S);
```

```
end Visto_2_op;
```

Arquivo UCF do 2º visto:

```
NET "A" LOC = "F3";
```

```
NET "B" LOC = "G3";
```

```
NET "C" LOC = "B4";
```

```
NET "E" LOC = "K3";
```

```
NET "F" LOC = "L3";
```

```
NET "G" LOC = "P11";
```

```
NET "S" LOC = "M5";
```